
REQUIREMENTS NOT MET

N/A

VIDEO FILE LINK

<https://youtube.com/shorts/4ubBHyGPA30?feature=share>

PROBLEMS ENCOUNTERED

The most significant problem I had was that I did not draw my breadboard properly since I forgot that the 74'00 and 74'02 chips count in a U pattern; thus, I had to redraw the wiring on my protoboard before I implemented the circuit on my real breadboard. Additionally, I was having difficulty inserting the switch chip into my board and accidentally broke two of the pins, requiring me to go to office hours to get a replacement part. Moreover, I was having slight difficulty understanding the mixed logic in the Quartus simulations until my PI explained it to me.

FUTURE WORK/APPLICATIONS

The concepts in this lab can be applied to designing control logic in embedded systems, especially when integrating components with different logic levels or optimizing for low power. These skills are also useful for building more complex digital circuits like decoders, multiplexers, and basic processors.

PRE-LAB QUESTIONS OR EXERCISES

N/A

PRE-LAB REQUIREMENTS (Design, Schematic, ASM Chart, VHDL, etc.)



Figure 1: Picture of contents from OOTB Complete EEL 3701 Kit

 


Figure 2: Parts received from Lab 0

LAB1A:

Equations:

$$V = \overline{[(A \cdot \overline{B}) + (C + \overline{D})]}$$

$$W = \overline{[(A \cdot \overline{B}) + (C + \overline{D})]}$$

 


Figure 3: Hand-Drawn Logic Diagram for Part A: $V = \overline{[(A \cdot \overline{B}) + (C + \overline{D})]}$ Using Only Positive-Logic AND, OR, and NOT Gates

1.2) Positive logic, only positive logic gates (No bubble on input pins)

$$W = \overline{[(A \cdot \overline{B}) + (C + \overline{D})]}$$

$$W = \overline{[(A \cdot \overline{B}) + (C + \overline{D})]}$$

 


Figure 4: Hand-Drawn Logic Diagram for Part A: $W = \overline{[(A \cdot \overline{B}) + (C + \overline{D})]}$ Using Positive Logic

Lab 1 Part 1.2 (Lab1a)
Name: Arion Stern
Class #: 10844
PI Name: Erick Zayas Ramos
Description: $W = \neg[(A * \neg B) + \neg(C + D)]$ (Positive Logic)

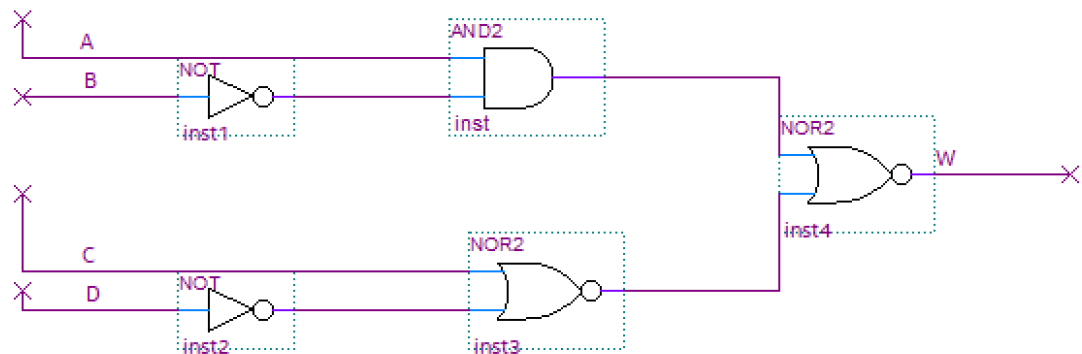
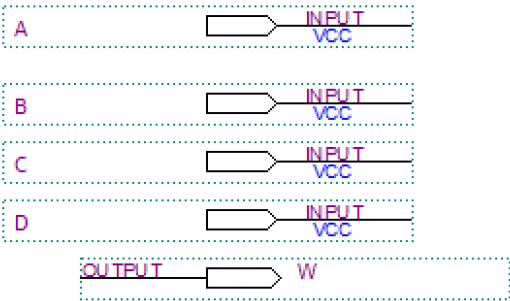


Figure 5: Quartus Schematic for Part A: $W = \neg[(A * \neg B) + \neg(C + D)]$

A	B	C	D	/B	A*/B	/D	C+/D	/(C+/D)	(A * /B) + /(C + /D)	W = /[(A * /B) + /(C + /D)]
0	0	0	0	1	0	1	1	0	0	1
0	0	0	1	1	0	0	0	1	1	0
0	0	1	0	1	0	1	1	0	0	1
0	0	1	1	1	0	0	1	0	0	1
0	1	0	0	0	0	1	1	0	0	1
0	1	0	1	0	0	0	0	1	1	0
0	1	1	0	0	0	1	1	0	0	1
0	1	1	1	0	0	0	1	0	0	1
1	0	0	0	1	1	1	1	0	1	0
1	0	0	1	1	1	0	0	1	1	0
1	0	1	0	1	1	1	1	0	1	0
1	0	1	1	1	1	0	1	0	1	0
1	1	0	0	0	0	1	1	0	0	1
1	1	0	1	0	0	0	0	1	1	0
1	1	1	0	0	0	1	1	0	0	1
1	1	1	1	0	0	0	1	0	0	1

Table 1: Truth Table for Part A: $W = \neg[(A * \neg B) + \neg(C + D)]$

A(H)	B(H)	C(H)	D(H)	W(H) = $\neg[(A * B) + (C + D)]$
L	L	L	L	H
L	L	L	H	L
L	L	H	L	H
L	L	H	H	H
L	H	L	L	H
L	H	L	H	L
L	H	H	L	H
L	H	H	H	H
H	L	L	L	L
H	L	L	H	L
H	L	H	L	L
H	L	H	H	L
H	H	L	L	H
H	H	L	H	L
H	H	H	L	H
H	H	H	H	H

Table 2: Voltage Table for Part A: $W = \neg[(A * B) + (C + D)]$

 


Figure 6: Annotated Timing Simulation for Part A equation W

LAB1B:

Equations:

$$X = \neg [(A \cdot \neg B) + \neg (C + \neg D)]$$

3.1) • Not limited in gate selection
• Choose activation levels to minimize gates

$$X = \neg [(A \cdot \neg B) + \neg (C + \neg D)]$$

$$X = \overline{(A \cdot \bar{B}) + \overline{C + \bar{D}}}$$

 


Figure 7: Hand-Drawn Mixed-Logic Diagram for Part B: $X = \neg [(A \cdot \neg B) + \neg (C + \neg D)]$

Lab 1 Part 3.1 (Lab1b)

Name: Arion Stern

Class #: 10844

PI Name: Erick Zayas Ramos

Description: $X = \neg [(A \cdot \neg B) + \neg (C + \neg D)]$ (Mixed Logic)

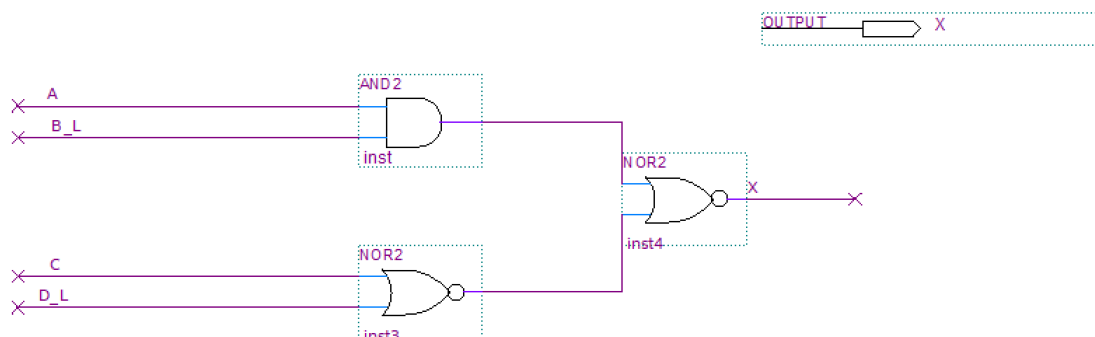


Figure 8: Quartus Schematic for Part B: $X = \neg [(A \cdot \neg B) + \neg (C + \neg D)]$

Lab 1 Report: Mixed-Logic Design and Quartus

A	B	C	D	/B	A*/B	/D	C+/D	/(C+/D)	(A * /B) + /(C + /D)	X = /[(A * /B) + /(C + /D)]
0	0	0	0	1	0	1	1	0	0	1
0	0	0	1	1	0	0	0	1	1	0
0	0	1	0	1	0	1	1	0	0	1
0	0	1	1	1	0	0	1	0	0	1
0	1	0	0	0	0	1	1	0	0	1
0	1	0	1	0	0	0	0	1	1	0
0	1	1	0	0	0	1	1	0	0	1
0	1	1	1	0	0	0	1	0	0	1
1	0	0	0	1	1	1	1	0	1	0
1	0	0	1	1	1	0	0	1	1	0
1	0	1	0	1	1	1	1	0	1	0
1	0	1	1	1	1	0	1	0	1	0
1	1	0	0	0	0	1	1	0	0	1
1	1	0	1	0	0	0	0	1	1	0
1	1	1	0	0	0	1	1	0	0	1
1	1	1	1	0	0	0	1	0	0	1

Table 3: Truth Table for Part B: $X = \text{NOT}[(A * \text{NOT} B) + \text{NOT}(C + \text{NOT} D)]$

A(H)	B(L)	C(H)	D(L)	X(H) = NOT [(A * NOT B) + NOT(C + NOT D)]
L	L	L	L	L
L	L	L	H	H
L	L	H	L	H
L	L	H	H	H
L	H	L	L	L
L	H	L	H	H
L	H	H	L	H
L	H	H	H	H
H	L	L	L	L
H	L	L	H	H
H	L	H	L	H
H	L	H	H	H
H	H	L	L	L
H	H	L	H	L
H	H	H	L	L
H	H	H	H	L

Table 4: Voltage Table for Part B: $X = \text{NOT}[(A * \text{NOT} B) + \text{NOT}(C + \text{NOT} D)]$

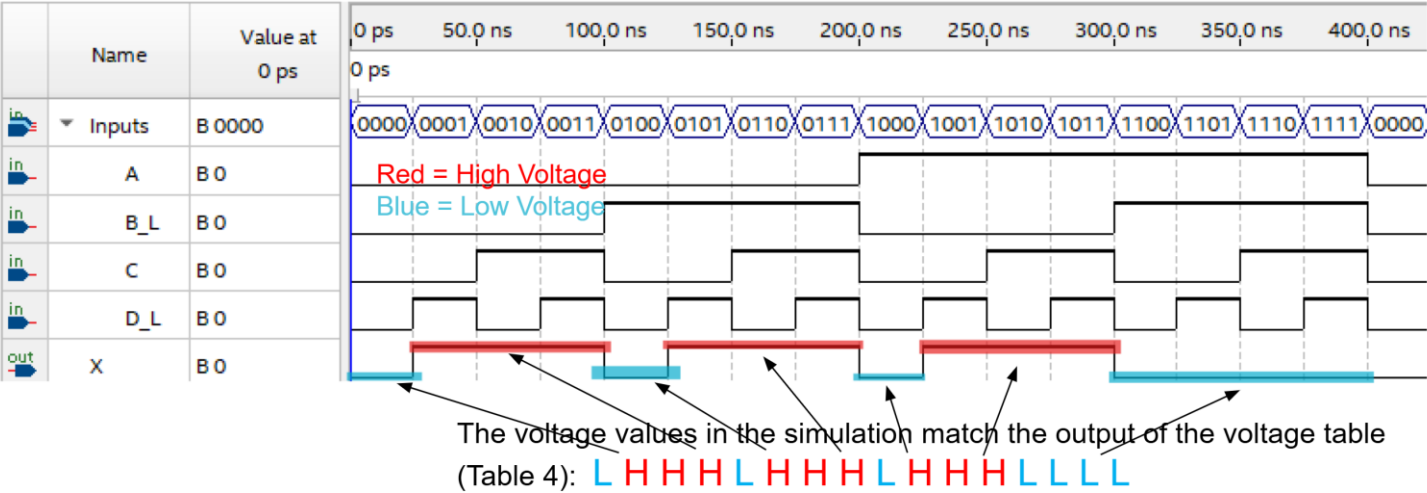


Figure 9: Annotated Quartus Simulation for Part B equation X

LAB1C:

Equations:

W = /[(A * /B) + /(C + /D)]

X = /[(A * /B) + /(C + /D)]

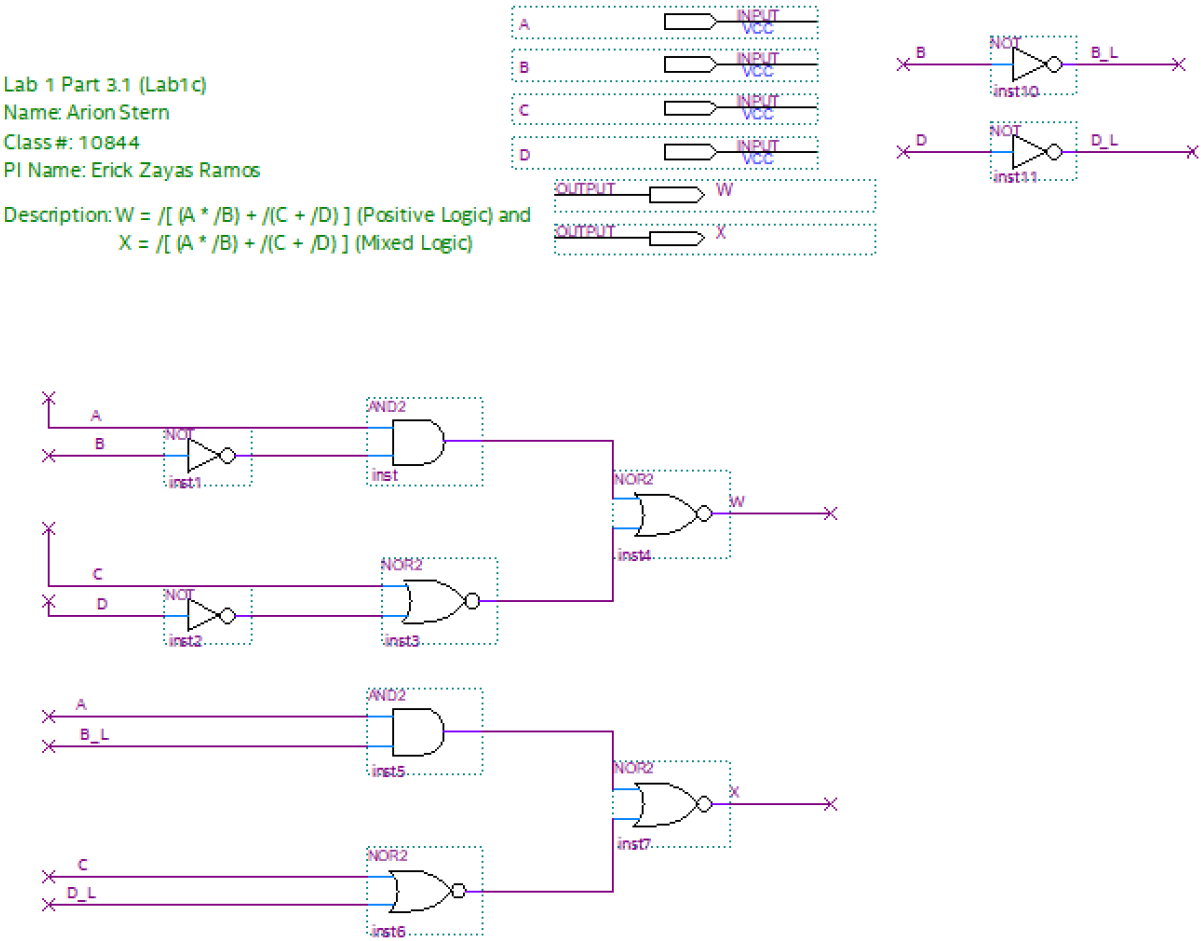


Figure 10: Combined Quartus Schematic for Part C: W and X Circuits (Top circuit depicts W and bottom depicts X)

 


Figure 11: Annotated Simulation for Part C: Comparing Outputs of W and X

LAB1D:

Equations:

$$Y = \overline{[(A \cdot \overline{B}) + \overline{(C + D)}]}$$

$$Z = [(A + \overline{B}) \cdot \overline{(C \cdot D)}]$$



5.1) 7 Gates 2 chips

• Y and Z have opposite active-low levels

• use 74'00 and 74'02

$$Y = \overline{[(A \cdot \overline{B}) + \overline{(C + D)}]}$$
  
$$Y = \overline{(A \cdot \overline{B}) + (C + \overline{D})}$$



$$Z = [(A + \overline{B}) \cdot \overline{(C \cdot D)}]$$

$$Z = (A + \overline{B}) \cdot (\overline{C \cdot D})$$

 


Figure 12: Hand-Drawn Mixed-Logic Schematic for Part D: equations Y and Z


Lab 1 Part 5.1 (Lab1d)

Name: Arion Stern


Class #: 10844

PI Name: Erick Zayas Ramos

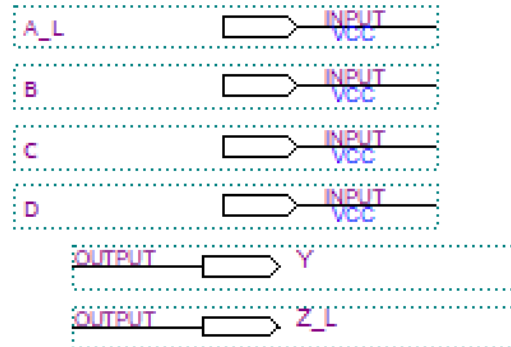Description: $Y = \neg[(A \cdot B) + \neg(C + D)]$ and
 $Z = [(A + B) \cdot \neg(C \cdot D)]$



$$Y = \neg[(A \cdot B) + \neg(C + D)]$$

 

$$Z = [(A + B) \cdot \neg(C \cdot D)]$$

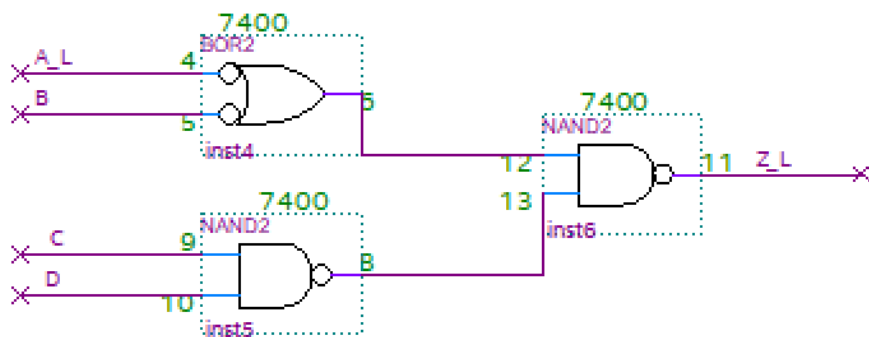


Figure 13: Quartus Schematic for Part D: Y and Z Circuits

A	B	C	D	/B	A*/B	/D	C+/D	/(C+/D)	(A * /B) + /(C + /D)	Y = /[(A * /B) + /(C + /D)]
0	0	0	0	1	0	1	1	0	0	1
0	0	0	1	1	0	0	0	1	1	0
0	0	1	0	1	0	1	1	0	0	1
0	0	1	1	1	0	0	1	0	0	1
0	1	0	0	0	0	1	1	0	0	1
0	1	0	1	0	0	0	0	1	1	0
0	1	1	0	0	0	1	1	0	0	1
0	1	1	1	0	0	0	1	0	0	1
1	0	0	0	1	1	1	1	0	1	0
1	0	0	1	1	1	0	0	1	1	0
1	0	1	0	1	1	1	1	0	1	0
1	0	1	1	1	1	0	1	0	1	0
1	1	0	0	0	0	1	1	0	0	1
1	1	0	1	0	0	0	0	1	1	0
1	1	1	0	0	0	1	1	0	0	1
1	1	1	1	0	0	0	1	0	0	1

Table 5: Truth Table for Part D: $Y = \text{/[(A * /B) + /(C + /D)]}$

A(L)	B(H)	C(H)	D(H)	Y(H) = /[(A * /B) + /(C + /D)]
L	L	L	L	L
L	L	L	H	L
L	L	H	L	L
L	L	H	H	L
L	H	L	L	H
L	H	L	H	L
L	H	H	L	H
L	H	H	H	H
H	L	L	L	H
H	L	L	H	L
H	L	H	L	H
H	L	H	H	H
H	H	L	L	H
H	H	L	H	L
H	H	H	L	H
H	H	H	H	H

Table 6: Voltage Table for Part D: $Y = \text{/[(A * /B) + /(C + /D)]}$


$$Z = [(A + /B) * /(C * D)]$$

A	B	C	D	/B	A + /B	C*D	/(C*D)	Z = [(A + /B) * /(C * D)]
0	0	0	0	1	1	0	1	1
0	0	0	1	1	1	0	1	1
0	0	1	0	1	1	0	1	1
0	0	1	1	1	1	1	0	0
0	1	0	0	0	0	0	1	0
0	1	0	1	0	0	0	1	0
0	1	1	0	0	0	0	1	0
0	1	1	1	0	0	1	0	0
1	0	0	0	1	1	0	1	1
1	0	0	1	1	1	0	1	1
1	0	1	0	1	1	0	1	1
1	0	1	1	1	1	1	0	0
1	1	0	0	0	1	0	1	1
1	1	0	1	0	1	0	1	1
1	1	1	0	0	1	0	1	1
1	1	1	1	0	1	1	0	0

Table 7: Truth Table for Part D: $Z = [(A + /B) * /(C * D)]$

A(L)	B(H)	C(H)	D(H)	Z(L) = [(A + /B) * /(C * D)]
L	L	L	L	L
L	L	L	H	L
L	L	H	L	L
L	L	H	H	H
L	H	L	L	L
L	H	L	H	L
L	H	H	L	L
L	H	H	H	H
H	L	L	L	L
H	L	L	H	L
H	L	H	L	L
H	L	H	H	H
H	H	L	L	H
H	H	L	H	H
H	H	H	L	H
H	H	H	H	H

Table 8: Voltage Table for Part D: $Z = [(A + /B) * /(C * D)]$

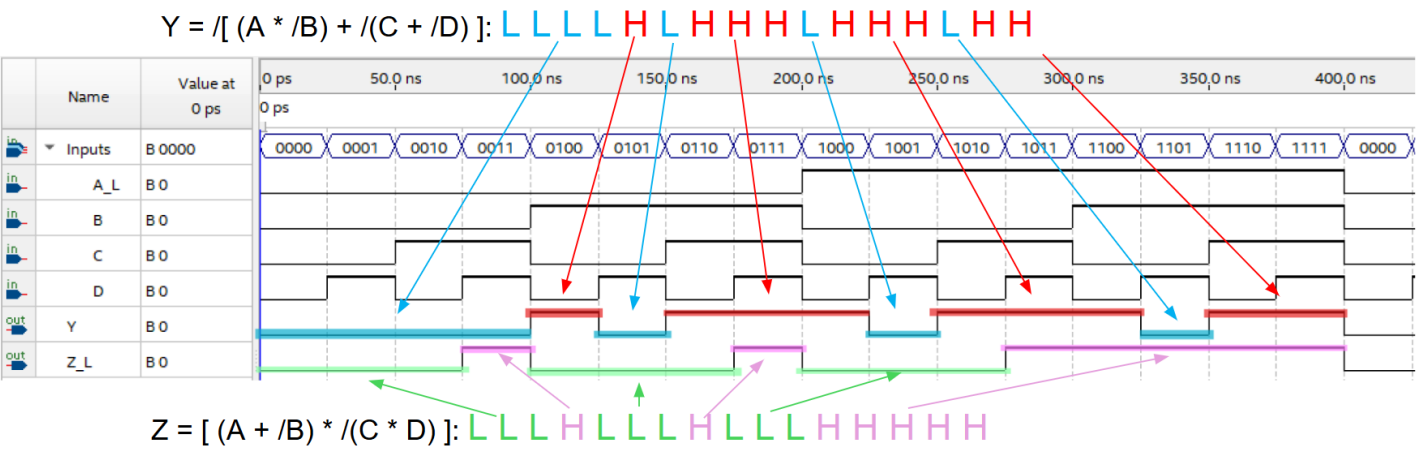

The voltage simulation verifies that both the equations were implemented correctly on quartus as they match the patterns from the voltage tables (Table 6 for the Y equation and Table 8 for the Z equation).

Figure 14: Annotated Quartus Simulation for Part D: Equations Y and Z

 


Figure 15: Breadboard Layout Diagram for Part D: Y and Z Circuits

Switch Legend:

 


Figure 16: Switch Legend Indicating ON Positions for Each Input for Part D

LED Legend:

 


Figure 17: LED Legend Showing DIP LED Positioning for Part D